
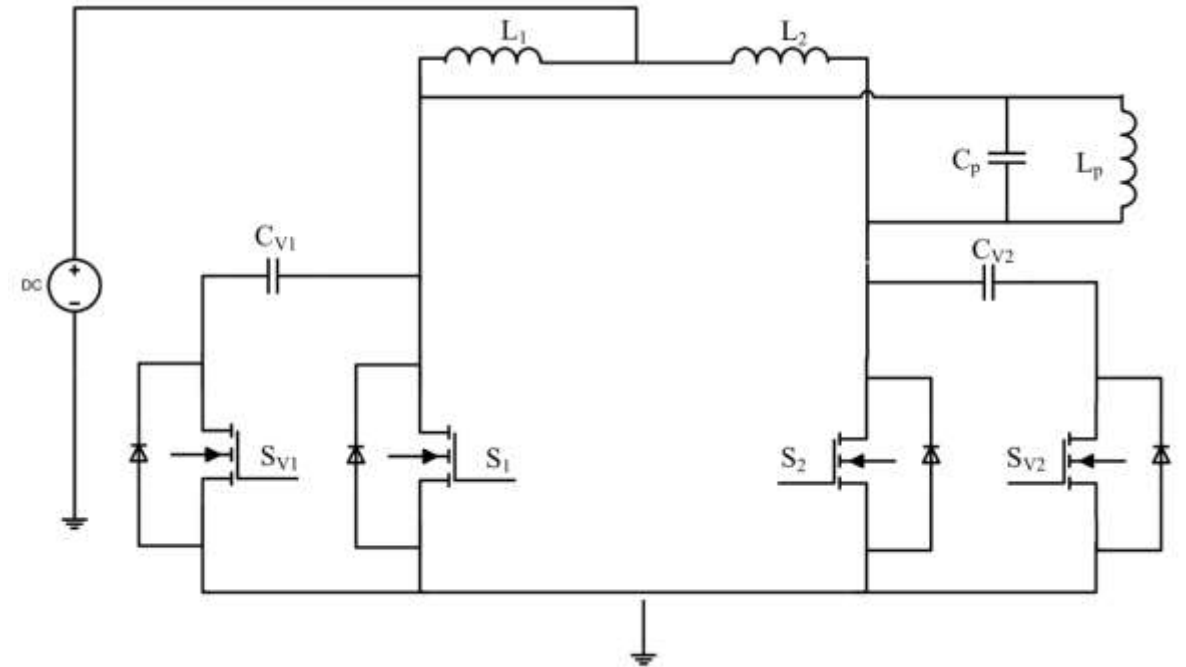


Current Fed Push Pull Converter

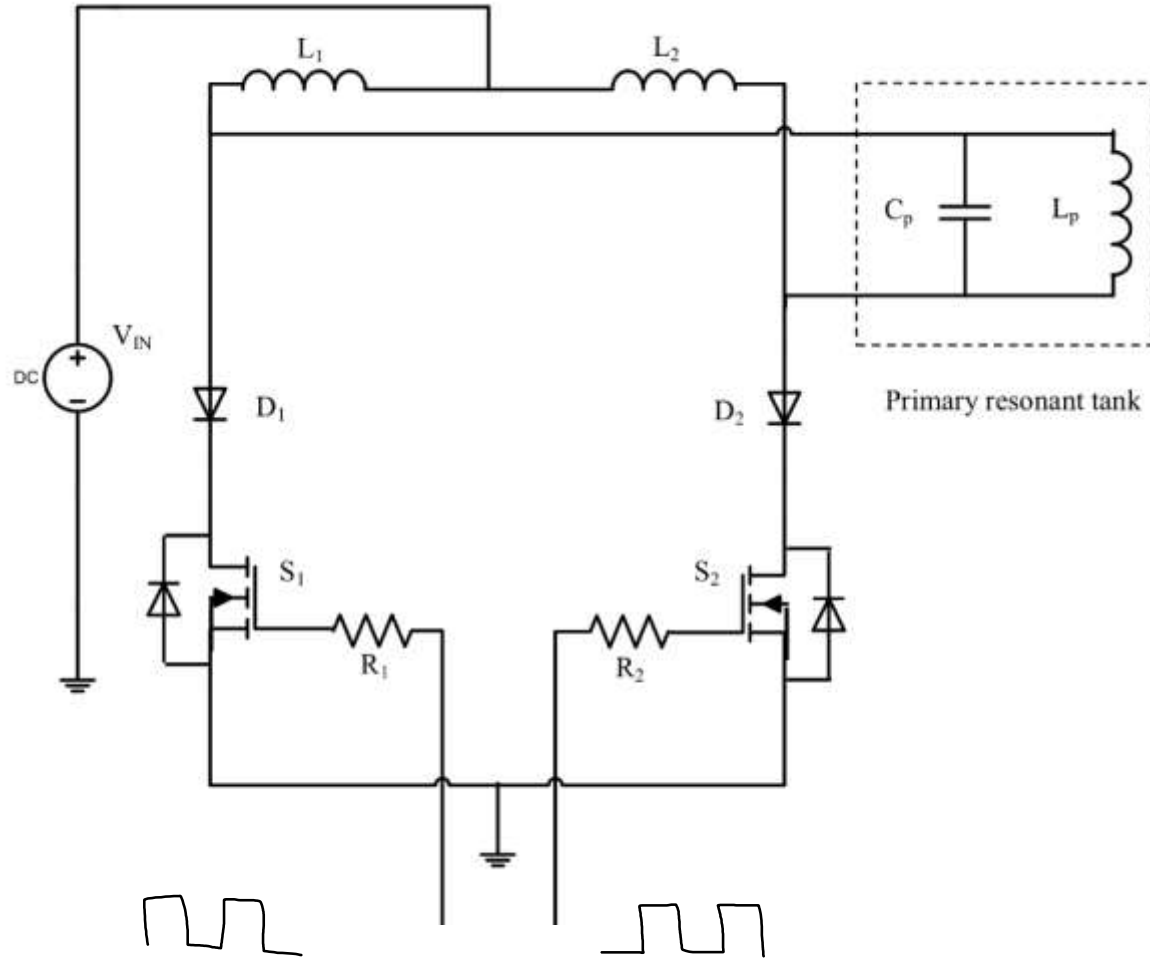


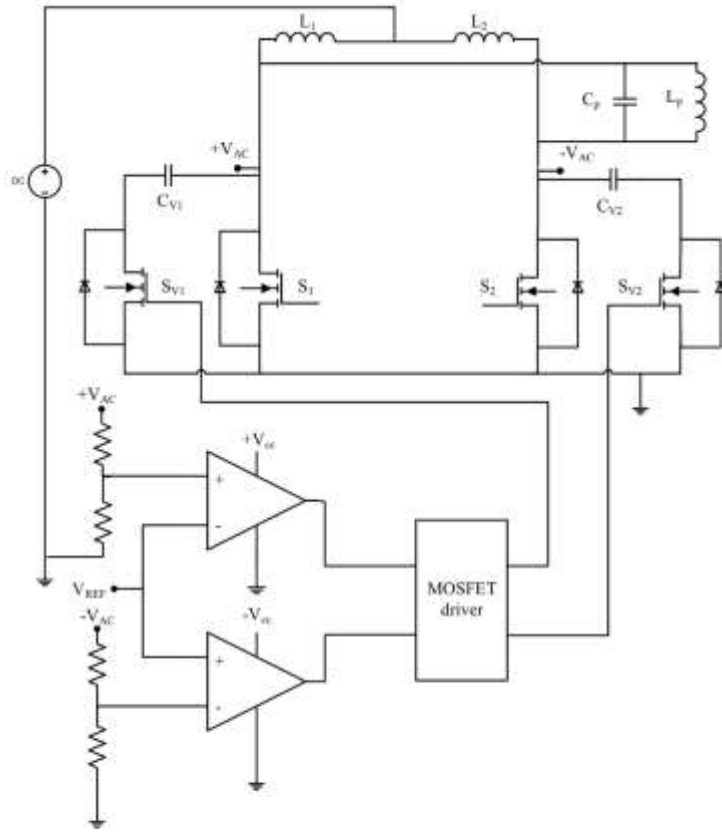


Figure 5-8: Frequency control circuitry of the system

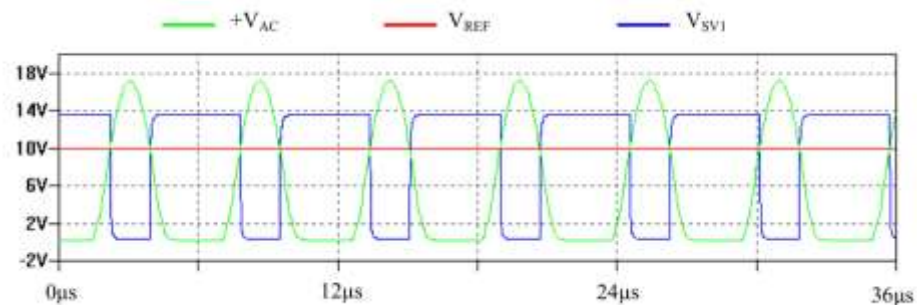

Last Week – frequency control circuitry

This week – steeper rise and fall, simulate MOSFET driver, connect Sv1 And Sv2 signals to gate

