


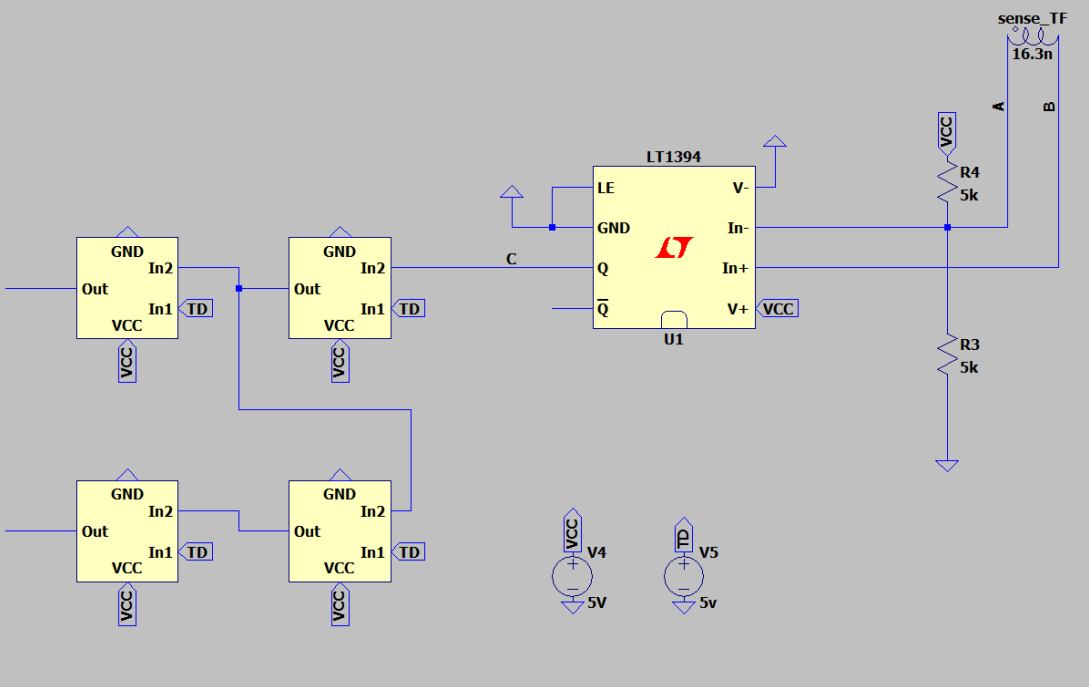


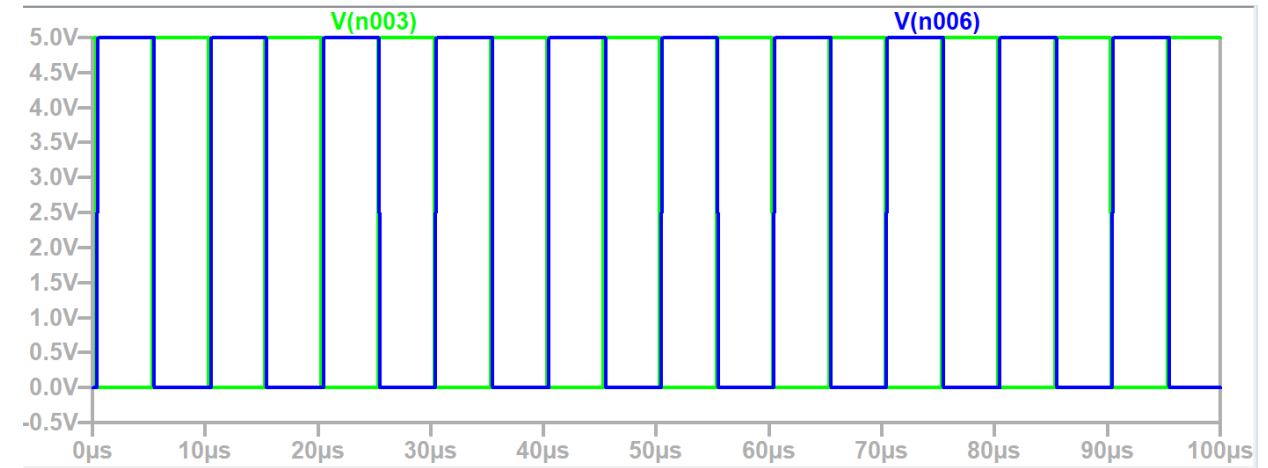

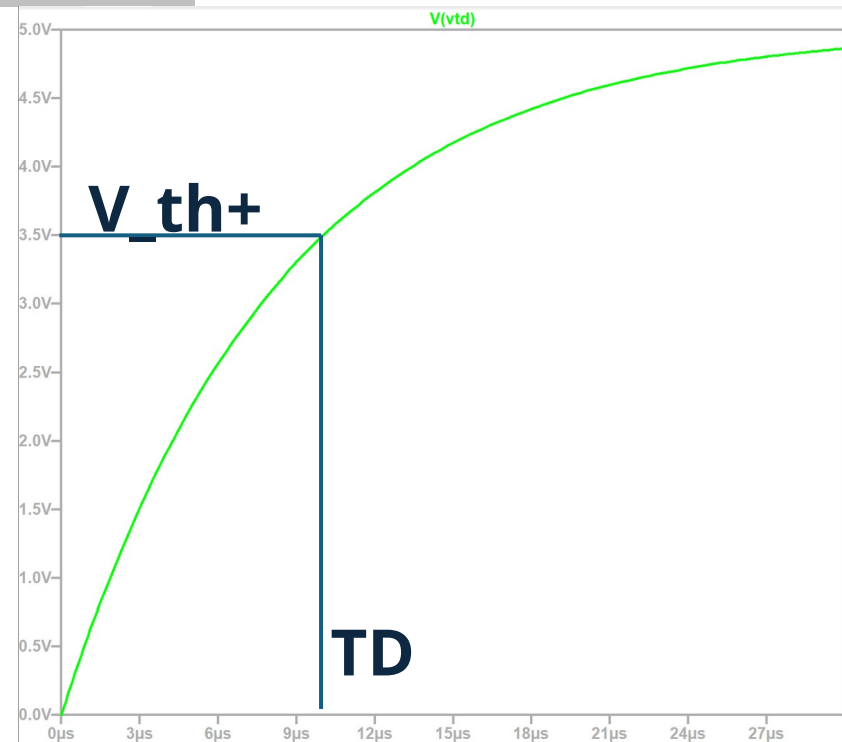Implemented real NAND gates using SPICE models found online



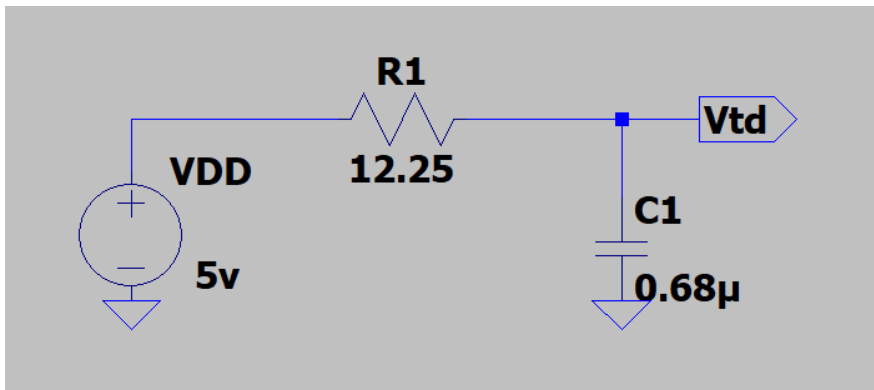Designed a method of obtaining the time delay signal for the NAND gates.



What's Next?

- Find an LTSpice model for an appropriate MOSFET driver
- Combine mine and Joe's circuit to test the full external circuitry with optimised component values