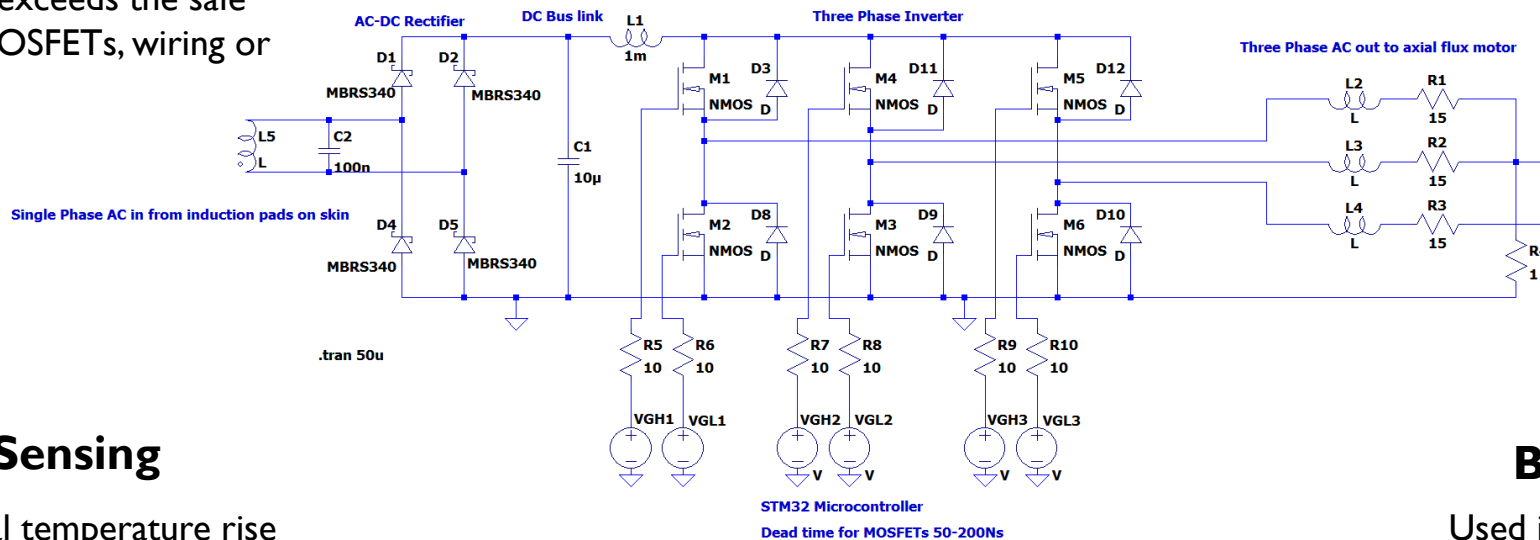


MOTOR CONTROL – SAFETY MEASURES

Current Sense Amplifier

Detects when current exceeds the safe rated limit of motor, MOSFETs, wiring or power supply.



Temperature Sensing

Need to limit internal temperature rise by reducing electrical load when temperature rises so system stays within thermal limits.

Gate Driver IC

Adds dead time so high-side and low-side MOSFETs aren't on at the same time otherwise it creates a direct short.

Bootstrap Capacitor

Used in half-bridge or full-bridge circuits and stores charge from driver supply which can be used to boost MOSFET gate above require voltage.